

Chapter 9

16/32-bit CPU Innovation Design



Architecture and Characteristics of KX9016

Ħ

 


Figure: The top-level structural diagram of 16-bit KX9016v1 CPU

 


Figure: The structural diagram of the top-level circuit of KX9016v1



Design of KX9016 Basic Hardware System

Module of One-step Beat Generation

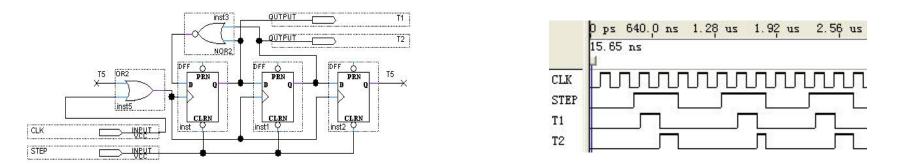


Figure: The circuit and its simulation waveform of beat pulse generator STEP2



ALU Module

```
module ALUV (input[15:0] a, b, input[3:0] sel, output reg [15:0] c);
  parameter alupass=0, andOp=1, orOp=2, notOp=3, xorOp=4, plus=5,
 alusub=6, inc=7, dec=8, zero=9;
  always @ (a or b or sel)
    case (sel)
       alupass : c <= a ;
                                   //Bus data is directly connected to ALU
         and Op : c \le a \& b;
                                   //Logic AND operation
         orOp : c <= a | b;
                                   //Logic OR operation
        xorOp : c \le a^b;
                                   //Logic XOR operation
                                   //Inverse operation
        notOp : c \leq a;
         plus : c \leq a + b;
                                   //Arithmetic addition operation
        alusub : c \leq a - b;
                                   //Arithmetic subtraction operation
           inc : c <= a + 1 ;
                                   //Adding 1 operation
           dec : c <= a - 1;
                                   //Subtracting 1 operation
                                   //Clearing the output
         zero : c <= 0 ;
       default : c \le 0 ;
   endcase
                  endmodule
```





Comparator Module

 



Figure: The module symbol of the comparator



```
module CMP V (input[15:0] a, b, input[2:0] sel, output reg compout);
 parameter eq=0, neq=1, gt=2, gt=3, lt=4, lte =5;
 always @ (a or b or sel)
   case (sel)
      eq : if (a==b) compout<=1; else compout<=0; // If a equals b, the output is 1
                                                   //otherwise the output is 0
      neq: if (a!=b) compout<=1; else compout<=0; // If a is not equal to b, the
                                                     //output is 1
      gt : if (a>b) compout<=1; else compout<=0; // If a is greater than b, the
                                                    //output is 1
      gte : if (a>=b) compout<=1; else compout<=0; //If a is not less than b, the
                                                     //output is 1
       lt : if (a<b) compout<=1; else compout<=0; //If a is less than b, the output</pre>
                                                    //is 1
      lte : if (a<=b) compout<=1; else compout<=0; //If a is not greater than b,</pre>
                                                     //the output is 1
     default :
                     compout<=0;
                endmodule
 endcase
```

Basic Register and Register Array

Basic register

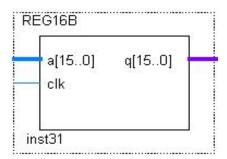

q[150]	a[150]
	ег
	clk
	rs

Figure: Basic register

Figure: Register containing three-state gate





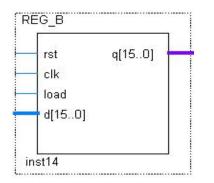


Figure: The register containing load enabling

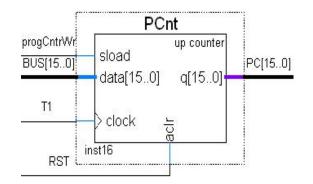


Figure: The alternative circuit of PC





```
module REG16B (input[15:0] a, input clk, output reg [15:0] q);
always@(posedge clk) q <= a; endmodule</pre>
```

```
REG_B.v
module REG_B (input rst, clk, load, input[15:0]d, output reg [15:0] q);
always @ (posedge clk or posedge rst)
if (rst==1'b1) q <= {16{1'b0}}; else
begin if (load == 1'b1) q <= d; end endmodule</pre>
```





Register array

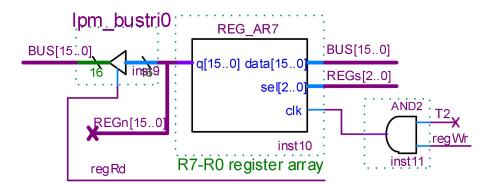


Figure: The register array element and the circuit of three-state control gate





```
module REG_AR7 (data, sel, clk, q);
input[15:0] data; input[2:0] sel; input clk; output[15:0] q;
reg[15:0] ramdata[0:7];
always @(posedge clk) ramdata[sel] <= data;
assign q = ramdata[sel]; endmodule
```





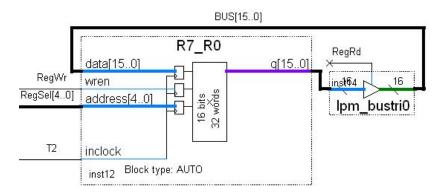


Figure: A circuit that uses LPM_RAM to replace a register array



Shifting Register Module

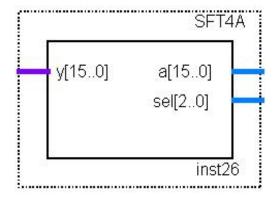


Figure: The shifter symbol



```
module SFT4A (input[15:0] a, input[2:0] sel, output reg[15:0] y);
    parameter shftpass=0, sftl=1, sftr=2, rotl=3, rotr=4;
    always @ (a or sel)
    case (sel)
    shftpass : y<=a ; //Data direct passing
    sftl : y<={a[14:0], 1'b0}; //left shift
    sftr : y<={1'b0, a[15:1]}; //right shift
    rotl : y<={a[14:0], a[15]}; // Circulatory left shift
    rotr : y<={a[0], a[15:1]}; // Circulatory right shift
    default : y<=0;
endcase endmodule</pre>
```



Design of KX9016v1 Instruction System

Instruction Format

Table	Single word instruction format

	Ope	ration	code			с с	Sou	rce oper code 2		Sou	rce oper code 1	ation	8,835	estinati operano	4
		Opcode	e					SRC	2		SRC			DST	
15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0



Table Double word instruction format

	•	ration o												estinati operano DST	5
15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
							16-bit	operan	d						
15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0

Table Double word instruction

Operation code					Destin	nation rand
0	0	1	0	0	0 0) 1

0	0	0	0	0	0	0	0	0	0	0	1	0	1	0	1
8	0				()				l	2			5	27



Instruction Operation Code

Table KX9016 preset instructions and their fu	unction table
---	---------------

Operation code	Instruction	Function	Operation code	Instruction	Function		
00000	NOP	Null operation	01111	IN	Peripheral data output instruction		
00001	LD	Loading data to registers	10000	JMPLTI	If less than, transferring to an immediate number address		
00010	STA	Storing the numbers of registers into memory	10001	JMPGT	If greater than, transferring		
00011	MOV	Transferring operands between registers	10010	OUT	Data output instruction		
00100	LDR	Loading the immediate number into the register	10011	MTAD	16-bit multiplicative accumulation		
00101	JMPI	Transferring to the address specified by an immediate number	10100	MULT	16-bit multiplication		
00110	JMPGTI	If greater than, transferring to the immediate number address	10101	JMP	Unconditional transferring		
00111	INC	After adding 1, putting back to the register	10110	JMPEQ	If equal, transferring		
01000	DEC	After subtracting 1, putting back to the register	10111	JMPEQI	If equal, transferring to an immediate number address		
01001	AND	AND operation between two registers	11000	DIV	32-bit Division		
01010	OR	OR operation between two registers	11001	JMPLTE	If not greater than transferring		
01011	XOR	XOR operation between two registers	11010	SHL	Left logical shift		
01100	NOT	NOT operation for the register	11011	SHR	Right logical shift		
01101	ADD	Addition operation for two registers	11100	ROTR	Circular right shift		
01110	SUB	Subtraction operation for two registers	11101	ROTL	Circular left shift		



Table Sample program

Instruction	Machine code	Word length	Operation code	Idle code	Source operand	Destination operand	Functional description		
LDR R1,0025H	2001H	2	00100	xxxxx	xxx	001	The immediate number		
LDR RI, 002511	0025H	ĩ		0000 000	00 0010 0101	1.	0025H is sent to R1		
LDD D2 0047U	2002H	2	00100	XXXXX	XXX	010	The immediate number		
LDR R2, 0047H	0047H	4		0000 00	0047H is sent to R2				
LDD D6 0026H	2006H	2	00100	xxxxx	XXX	110	The immediate number		
LDR R6, 0036H	0036H	2		0000 000	00 0011 0110)	0036H is sent to R6		
LD R3, [R1]	080BH	1	00001	xxxxx	001	011	Taking the number from the RAM storage unit specified by R1 to R3		
STA [R2], R3	101AH	1	00010	xxxxx	011	010	Saving the content of R3 into the RAM unit specified by R2		
JMPGTI 0000H	300EH	2	00110	XXXXX	001	110	If R1>R6,transferring to		
	0000H	-		000000	0000000000	<u>(-</u>	address [0000H]		
INC R1	3801H	1	00111	XXXXX	XXX	010	R1+1 ? R1		
INC R2	3802H	1	00111	XXXXX	xxx	010	R2+1 ? R2		
JMPI 0006H	2800H 0006H	2	00101	xxxxx	xxx	xxx	Absolute address transferring instruction: transferring to address 0006H		



Example of Software Program Design

Address	Operation code	Instruction	Functional description
0000H 0001H	2001H 0032H	LDR R1,0032H	Sending the immediate number of 0032H to the register R1
0002H 0003H	2002H 0011H	LDR R2,0011H	Sending the immediate number of 0011H to the register R2
0004H 680AH ADD R1, R2		ADD R1, R2, R3	Sending the addition of the contents of the registers R1 and R2 to R3
0005H	1819H	MOV R1, R3	Sending the contents of the register R3 into the R1
0006H	3802H	INC R2	R2+1→R2
0007H	101AH	STA [R2], R3	Saving the content of the R3 into the RAM uni of the R2 specified address
0008H	080BH	LD R3, [R1]	Sending the data of the RAM unit of the R specified address to R3
0009H	0000H	NOP	Null operation

Table The example of the assembler program of 7 instructions



TableThe contents of the	memory initialization file l	RAM_16.mif	
WIDTH = 16;	03 :0011;	0B :0000;	13 :0000;
DEPTH = 256;	04 :680A;	0C :0000;	
ADDRESS_RADIX = HEX;	05 :1819;	0D :0000;	41 :0000;
DATA_RADIX = HEX;	06 :3802;	0E :0000;	42 :0000;
CONTENT BEGIN	07 :101A;	0F :0000;	43 :A6C7;
00 :2001;	08 :080B;	10 :0000;	1000
01 :0032;	09 :0000;	11 :0000;	4F :0000;
02 :2002;	0A :0000;	12 :1524;	END;

Design of KX9016 Controller



9016 C'ontr	oller
	et, instrReg, compout, progCntrWr, progCntrRd,
	tRegWr, outRegRd, shiftSel, aluSel, compSel,
	r, regSel, regRd, regWr, rw, vma);
input clock; input r	
	.nput compout;// The input of instruction register operation
	//code and input of comparator result
output progCntrWr;	<pre>// Program register synchronous loading allowing,</pre>
	<pre>//but the rising edge of T1 is required to be</pre>
	//effective.
output progCntrRd;	// Program register data is output to bus three-state
	//switch allowing control
output addrRegWr;	<pre>// The address register allows bus data to lock in, but</pre>
	//it needs T2 to be effective
output addrRegRd;	<pre>// Address register read bus allowing // Output registers allow bus data to be written, but</pre>
output outRegWr;	<pre>// output registers allow bus data to be written, but //it needs T2 to be effective</pre>
output outRegRd;	<pre>// The allowing of the output register data to enter</pre>
the	<pre>//bus, that is, to open the three-state gate</pre>
	output[3:0] aluSel; // Function selection of shifter and //ALU
output[2:0] compSel;	output opRegRd; // Function selection of comparator and
	<pre>//readout allowing of working register</pre>
output opRegWr;	// Bus data is allowed to be locked into the work
	<pre>//registers,but T1 is required to be effective</pre>
output instrWr;	//Bus data is allowed to be locked into instruction
	//register, but T2 is required to be effective
output[2:0] regSel;	<pre>//Register array selection</pre>
output regRd;	<pre>// Register array data is output to bus three-state switch //allowing control</pre>
output regWr;	<pre>//allowing control // Data on bus is allowed to write to register array,</pre>
output regar,	<pre>// but it needs T2 to be effective.</pre>
output rw;	<pre>//rw=1, RAM write allowing; rw=0, RAM read allowing</pre>
output vma;	// Memory RAM data is output to bus three-state switch
	//allowing control
reg progCntrWr, progCr	trRd, addrRegWr, addrRegRd, outRegWr, outRegRd,
opRegRd, opRegWr,	instrWr, regRd, vma, regWr, rw;
	<pre>Sel; wire[2:0] compSel; reg[3:0] aluSel;</pre>
parameter shftpass=0,	alupass=0, zero=9, inc=7, plus=5 ;//Seeing example 8-1
	//for reference
	eset2=1, reset3=2, execute=3, nop=4, load=5, store=6,
	<pre>1=9, store2=10, store3=11, store4=12,incPc=13, adI2=19,loadI3=20,loadI4=21,loadI5=22,loadI6=23, inc2=24</pre>
	=27, move2=28, add2=29, add3=30, add4=31;
	state variable elements for microoperation, namely add2,
	added to the state machine
	e, next state; // Definition of current and next
	//state variables
always @(current_state or	instrReg or compout) begin :COM//Combinational process
progCntrWr<=0; progCntrF	d<=0; addrRegWr<=0; addrRegRd<=0; outRegWr<=0;
	hftpass; aluSel<=alupass; opRegRd<=0; opRegWr<=0;
	regRd<=0;
case (current_state)	
	Sel<=zero; shiftSel<=shftpass;
	1'b1; next_state<=reset2; end
	RegRd<=1'b1; progCntrWr<=1'b1; <=1'b1; next state<=reset3; end
	<=1'b1; rw<=1'b0; instrWr<=1'b1;
resets . segin Villa	, in a woy and chief a with

end

next state<=execute;</pre>



Timing Simulation and Hardware Testing of KX9016

Timing Simulation and Waveform Analysis of Instruction Execution

 


Figure: KX9016 simulation waveform, which includes the timing of ADD command and MOV command

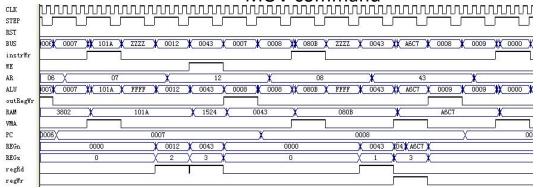


Figure: KX9016 simulation waveform, which includes the timing of STA command and LD command



Hardware Testing of CPU Operation Condition

Instance

Status

 


Figure: The circuit scheme for adding phase-locked loop

CPU	16B	Waiting for trig	iger	1385 cells	11264 bits	0 blocks	3 blocks	0 blocks
log: 2	012/03	/24 21:36:09 #0					click	to insert time bar
Туре	Alias	Name	-16	-8 0	8	16 24	32 40	48 56
		⊕- ALU	(0012h				0043h
								12h
		⊕- BUS		0012h				0043h
		€- PC						0007h
0	, j	⊕- RAM		101Ah)				1524h
		⊕- REGn	0	0012h X				0043h
0		WE						

M512,MLAB: 0/0

M4K,M9K: 4/260

M-RAM,M144K: 0/0

LEs: 1385 Memory: 11264

Figure: SignalTap II executes real-time test waveform for KX9016 to write data instructions from RAM



🚗 0 🛛 RA	.M8:															
000000	20 01	00 32	20 02	00 11	68 OA	18 19	38 02	10 1A	08 0B	00 00	00 00	00 00	00 00	00 00	00 00	00 00
000010	00 00	00 00	00 43	00 00	00 00	00 00	00 00	00 00	00 00	00 00	00 00	B3 B4	B5 B6	B7 B8	D1 D2	D3 D4
000020	D5 D6	D7 D8	D9 DA	E1 E2	E3 E4	E5 E6	20 08	20 09	20 OA	20 OB	20 OC	20 OD	20 OE	20 OF	20 10	20 11
000030	D5 D6	D7 D8	D1 23	E1 E2	E3 E4	E5 E6	20 08	20 09	20 OA	20 OB	20 OC	00 00	00 00	00 00	00 00	00 00
000040	00 00	00 00	00 00	A6 C7	00 00	00 00	00 00	00 00	00 00	00 00	00 00	00 00	00 00	00 00	00 00	00 00

Figure: The testing of the change of RAM data in KX9016 by In-System Memory Content Editor

 


Figure: The connection of the S/P module to the KX9016 port





* *	WE	0						
**		Oh			Oh		(2h	3h
**		08h	06h	X	07h		(12h
**		0008h	00	07h) 101Ah	FFFFh	0012h	0043h
**		0000h			0000h		0012h	0043h
**		0008h	0006h	χ		000)7h	
**	⊕ RAM[150]	0043h	38	102h	χ	101Ah		1524h

Figure: The real-time testing waveform of the in-system S/P module executing STA data writing instructions from RAM for KX9016

Examples of Application Program Design and System Optimization of KX9016

Multiplication Algorithm and Its Hardware Implementation

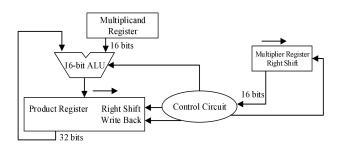


Figure: The hardware implementation of multiplication algorithm 1

 


Figure: The hardware implementation of the improved multiplication algorithm 2



 


Figure: The flow chart of the multiplication algorithm 1

Figure: The flow chart of the multiplication algorithm 2





Division Algorithm and Its Hardware Implementation

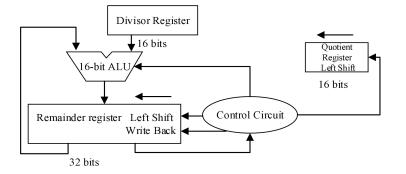


Figure: The hardware structure of division algorithm 1

 


Figure: The hardware structure of division algorithm 2





Optimization of KX9016v1 Hardware System



Design of 32-bit RISC-V Processor

RISC-V Basic Structure and Basic Integer Instruction Set RV32I

Format	Meaning		31~26	25~20	19~15	14~12	11	~7	6~0
R-type	Register	. st	funct7	rs2	rsl	funct3	r	d	opcode
I-type	Immediate		imm[11:0]		rs1	funct3	r	opcode	
S-type	Store	im	m[11:5]	rs2	rs1	funct3	imm	[4:0]	opcode
B-type	Branch	imm[12]	imm[10:5]	rs2	rsl	funct3	imm[4:1]	imm[11]	opcode
U-type	Upper Immediate		im	m[31:12]			r	d	opcode
J-type	Jump	imm[20]	imm[10:1]	imm[11]	imm[19:12]	r	d	opcode

Table	Types and	formats of RV32	I instructions
-------	-----------	-----------------	----------------



Table RV32I general Register

Index	Name	Alias	Function
R0	x 0	zero	Hardwired zero
R1	x1	ra	Return address
R2	x2	sp	Stack pointer
R3	x3	gp	Global pointer
R4	x4	tp	Thread pointer
R5~R7	x5~x7	t0~t2	Temporary
R8	x8	s0/fp	Saved register, frame pointer
R9	x9	s1	Saved register
R10~R11	x10~x11	a0~a1	Function argument, return value
R12~R17	x12~x17	a2~a7	Function argument
R18~R27	x18~x27	s2~s11	Saved register
R28~R31	x28~x31	t3~t6	Temporary



Table	RV32I basic integer instruction set
Labie	Ry521 basic integer insu action set

RV32I Base	Format	Opcode	funct7	funct3	Other	Function
SLL rd,rs1,rs2	R	0110011	0000000	001		Shift Left Logical
SLLI rd.rs1.shamt	I	0010011	0000000	001		Shift Left Log. Imm.
SRL rdrs1.rs2	R	0110011	0000000	101		Shift Right Logical
SRLI rd.rs1,shamt	I	0010011	0000000	101		Shift Right Log. Imm.
SRA rd,rs1,rs2	R	0110011	0100000	101		Shift Right Arithmetic
SRAI rs.rs1.shamt	I	0010011	0100000	101		Shift Right Arith. Imm.
ADD rd.rs1.rs2	R	0110011	0000000	000		ADD
ADDI rd,rs1,imm	I	0010011		000		ADD Immediate
SUB rd.rs1.rs2	R	0110011	0100000	000		SUBtract
LUI rd.imm	U	0110111				Load Upper Imm
AUIPC rd,imm	U	0010111			-	Add Upper Imm to PC
XOR rd,rs1,rs2	R	0110011	0000000	100		XOR
XORI rd,rs1,imm	I	0010011		100		XOR Immediate
OR rd,rs1,rs2	R	0110011	0000000	110		OR
ORI rd,rs1,imm	I	0010011		110		OR Immediate
AND rd,rs1,rs2	R	0110011	0000000	111		AND
ANDI rd,rs1,imm	I	0010011		111	-	AND Immediate
SLT rd,rs1,rs2	R	0110011	0000000	010	ľ	Set <
SLTI rd,rs1,imm	I	0010011		010		Set < Immediate
SLTU rd,rs1,rs2	R	0110011	0000000	011		Set < Unsigned
SLTIU rd,rs1,imm	I	0010011		011		Set < Imm Unsigned
BEQ rs1,rs2,imm	В	1100011		000	-	Branch =
BNE rs1,rs2,imm	B	1100011		001	-	Branch ?
BLT rs1,rs2,imm	B	1100011	1. 	100		Branch <
BGE rs1,rs2,imm	В	1100011	12-2-1	101		Branch ≥
BLTU rs1,rs2,imm	В	1100011		110	-	Branch < Unsigned
BGEU rs1,rs2,imm	В	1100011		111	-	Branch = Unsigned
JAL rd,imm	J	1101111				J&L
JALR rd,rs1,imm	I	1100111		000		Jump & Link Register
FENCE	I	0001111		000	0	Synch thread
FENCE.I	I	0001111	()	001	1	Synch Instr & Data
ECALL	I	1110011		000	0	CALL
EBREAK	Ι	1110011		000	1	BREAK



32-bit Multiplication Instruction Set RV32M

Category	RV32M(Multiply-Divide)	Format	Opcode funct Fuction
	MUL rd,rs1,rs2	R	MULtiply
10101	MULH rd,rs1,rs2	R	MULtiply High
Multiply	MULHSU rd,rs1,rs2	R	MULtiply High Sign/Uns
	MULHU rd,rs1,rs2	R	MULtiply High Uns
D' 11	DIV rd,rs1,rs2	R	DIVide
Divide	DIVU rd,rs1,rs2	R	DIVide Unsigned
D 1	REM rd,rs1,rs2	R	REMainder
Remainder	REMU rd,rs1,rs2	R	REMainder Unsigned

Table RV32M integer multiplication and division instruction set



16-bit Compressed Instruction Set RVC

Format	Meaning	15~13	12	11	10~6	5	4~2	1~0
CR	Register	func	t4	r	d/1s1	rs	2	op
CI	Immediate	funct3	imm	r	d/rs1	im	m	op
CSS	Stack-relative Store	funct3	imm		rs2'		op	
CIW	Wide Immediate	funct3		i	imm		rd'	op
CL	Load	funct3	imn	n	rs1'	imm	rd'	op
CS	Store	funct3	imn	n	rs1'	imm	rs2'	op
СВ	Branch	funct3	offse	et	rs1'	off	set	op
CJ	Jump	funct3			Jump targ	et		ор

Table Types and Formats of RVC Instructions



Table Part of RVC and the comparison with 32-bit instructions

	RVC	RISC	C-V equivalent	Funciton	
C.LW	rd',rs1',imm	LW	rd',rs1',imm*4	Load Word	
C.LWSP	rd,imm	LW	rd,sp,imm*4	Load Word SP	
C. <mark>S</mark> W	rs1',rs2',imm	SW	rs1',rs2',imm*4	Store Word	
C.SWSP	rs2,imm	SW	rs2,sp,imm*4	Store Word SP	
C.ADD	rd,rs1	ADD	rd,rd,rs1	ADD	
C.ANDI	rd,imm	ANDI	rd,rd,imm	AND Immediate	
C.OR	rd,rs1	OR	rd,rd,rs1	OR	
C.XOR	rd,rs1	AND	rd,rd,rs1	Exclusive OR	